

ENGR

2405

Chapter 8

Second

Order

Circuits


Overview

- **The previous chapter introduced the concept of first order circuits.**
- **This chapter will expand on that with second order circuits: those that need a second order differential equation.**
- **RLC series and parallel circuits will be discussed in this context.**
- **The step response of these circuits will be covered as well.**
- **Finally the concept of duality will be discussed.**


Second Order Circuits

- The previous chapter considered circuits which only required first order differential equations to solve.
- However, when more than one “storage element”, *i.e.* capacitor or inductor is present, the equations require second order differential equations
- The analysis is similar to what was done with first order circuits
- This time, though we will only consider DC independent sources

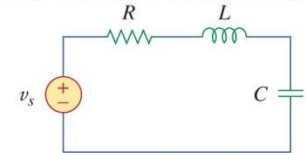
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




(a)

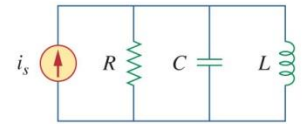

(b)

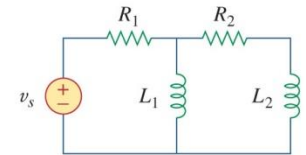

(c)

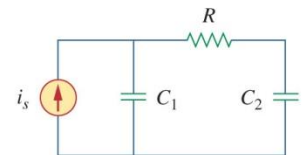

(d)

Finding Initial and Final Values

- Working on second order system is harder than first order in terms of finding initial and final conditions.
- You need to know the derivatives, dv/dt and di/dt as well.
- Getting the polarity across a capacitor and the direction of current through an inductor is critical.
- Capacitor voltage and inductor current are always continuous.


Source Free Series RLC

- Consider the circuit shown.
- The energy at $t=0$ is stored in the capacitor, represented by V_0 and in the inductor, represented by I_0 .

$$v(0) = \frac{1}{C} \int_{-\infty}^0 i dt = V_0$$

$$i(0) = I_0$$

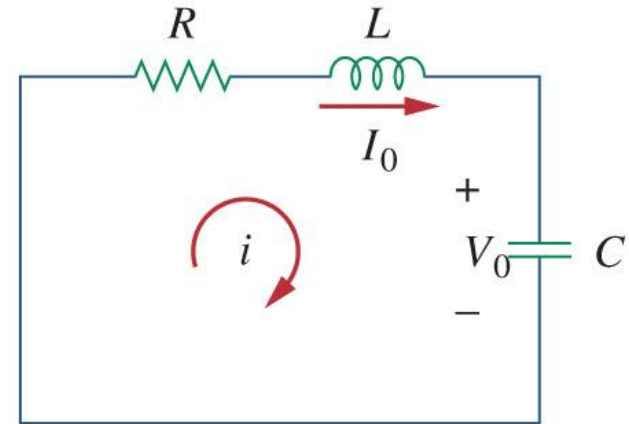Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Source Free Series RLC

- **Applying KVL around the loop:**

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = 0$$

- **The integral can be eliminated by differentiation:**

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

- **Here you can see the second order equation that results**

Source Free Series RLC

- **Two initial conditions are needed for solving this problem.**
- **The initial current is given.**
- **The first derivative of the current can also be had:**

$$Ri(0) + L \frac{di(0)}{dt} + V_0 = 0$$

- **Or**

$$\frac{di(0)}{dt} = -\frac{1}{L}(RI_0 + V_0)$$

Source Free Series RLC

- Based on the first order solutions, we can expect that the solution will be in exponential form.
- The equation will then be:

$$Ae^{st} \left(s^2 + \frac{R}{L}s + \frac{1}{LC} \right) = 0$$

- For which the solutions are:

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$


Overdamped ($\alpha > \omega_0$)

- When $\alpha > \omega_0$, the system is overdamped
- In this case, both s_1 and s_2 are real and negative.
- The response of the system is:

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

- From this, we should not expect to see an oscillation

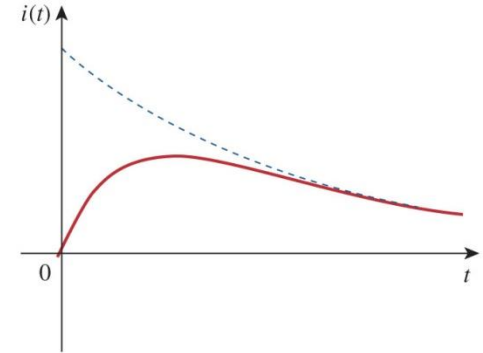Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

Critically Damped ($\alpha=\omega_0$)


- When $\alpha=\omega_0$, the system is critically damped.
- The differential equation becomes:

$$\frac{d}{dt}(e^{\alpha t}i) = A_1$$

- For which the solution is:

$$i(t) = (A_2 + A_1 t)e^{-\alpha t}$$

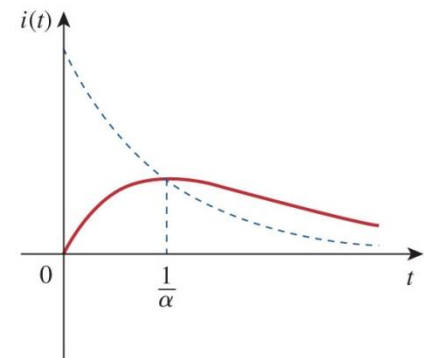- There are two components to the response, an exponential decay and an exponential decay multiplied by a linear term



(b)

Underdamped ($\alpha < \omega_0$)

- When $\alpha < \omega_0$, the system is considered to be underdamped
- In this case, the solution will be:

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

- Where $j = \sqrt{-1}$ and $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$
- ω_0 is often called the undamped natural frequency
- ω_d is called the damped natural frequency

Damping and RLC networks


- **RLC networks can be characterized by the following:**
 - 1. The behavior of these networks is captured by the idea of damping**
 - 2. Oscillatory response is possible due to the presence of two types of energy storage elements.**
 - 3. It is typically difficult to tell the difference between damped and critically damped responses.**

Source Free Parallel RLC Network

- Now let us look at parallel forms of RLC networks
- Consider the circuit shown
- Assume the initial current and voltage to be:

$$i(0) = I_0 = \frac{1}{L} \int_{-\infty}^0 v(t) dt$$

$$v(0) = V_0$$

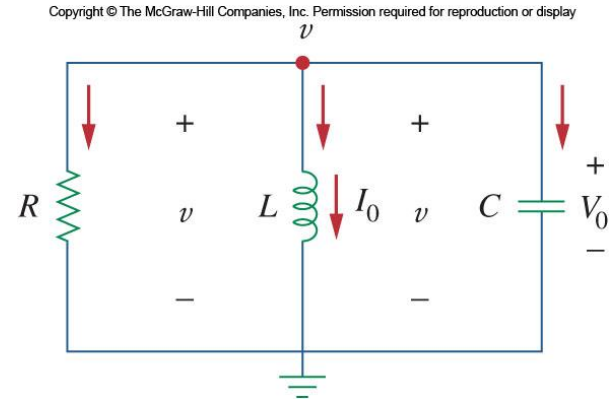

Source Free Parallel RLC Network

- **Applying KCL to the top node we get:**

$$\frac{v}{R} + \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau + C \frac{dv}{dt} = 0$$

- **Taking the derivative with respect to t gives:**

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

- **The characteristic equation for this is:**

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

Source Free Parallel RLC Network

- From this, we can find the roots of the characteristic equation to be:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$
$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

- As in last time, there are three scenarios to consider.

Damping

- **For the overdamped case, the roots are real and negative, so the response is:**

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

- **For critically damped, the roots are real and equal, so the response is:**

$$v(t) = (A_2 + A_1 t) e^{-\alpha t}$$

Underdamped

- In the underdamped case, the roots are complex and so the response will be:

$$v(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

- To get the values for the constants, we need to know $v(0)$ and $dv(0)/dt$.
- To find the second term, we use:

$$\frac{V_0}{R} + I_0 + C \frac{dv(0)}{dt} = 0$$

Underdamped

- **The voltage waveforms will be similar to those shown for the series network.**
- **Note that in the series network, we first found the inductor current and then solved for the rest from that.**
- **Here we start with the capacitor voltage and similarly, solve for the other variables from that.**


Step Response of a Series RLC Circuit

- Now let us consider what happens when a DC voltage is suddenly applied to a second order circuit.
- Consider the circuit shown. The switch closes at $t=0$.
- Applying KVL around the loop for $t>0$:

$$L \frac{di}{dt} + Ri + v = V_s$$

- **but**

$$i = C \frac{dv}{dt}$$

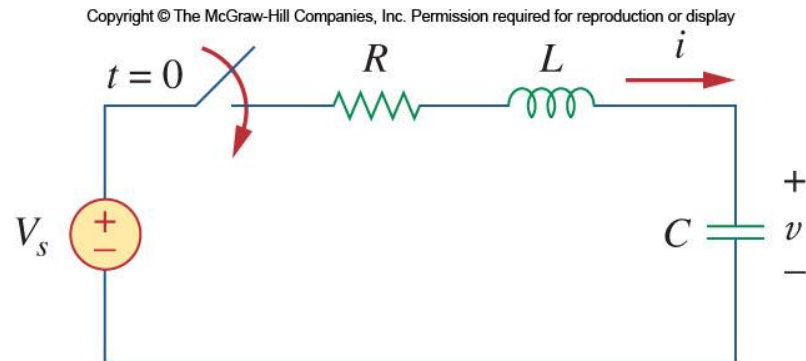

Step Response of a Series RLC Circuit

- **Substituting for i gives:**

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC}$$

- **This is similar to the response for the source free version of the series circuit, except the variable is different.**
- **The solution to this equation is a combination of transient response and steady state**

$$v(t) = v_t(t) + v_{ss}(t)$$

Step Response of a Series RLC Circuit

- The transient response is in the same form as the solutions for the source free version.
- The steady state response is the final value of $v(t)$. In this case, the capacitor voltage will equal the source voltage.

Step Response of a Series RLC Circuit

- The complete solutions for the three conditions of damping are:

$$v(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$v(t) = V_s + (A_1 + A_2) e^{-\alpha t} \quad (\text{Critically Damped})$$

$$v(t) = V_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) \quad (\text{Underdamped})$$

- The variables A_1 and A_2 are obtained from the initial conditions, $v(0)$ and $dv(0)/dt$.

Step Response of a Parallel RLC Circuit

- The same treatment given to the parallel RLC circuit yields the same result.
- The response is a combination of transient and steady state responses:

$$i(t) = I_s + A_1 e^{\tau_1 t} + A_2 e^{\tau_2 t} \quad (\text{Overdamped})$$

$$i(t) = I_s + (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically Damped})$$

$$i(t) = I_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$

- Here the variables A_1 and A_2 are obtained from the initial conditions, $i(0)$ and $di(0)/dt$.

General Second Order Circuits

- The principles of the approach to solving the series and parallel forms of RLC circuits can be applied to second order circuits in general:
- The following four steps need to be taken:
 1. First determine the initial conditions, $x(0)$ and $dx(0)/dt$.

Second Order Op-amp Circuits

2. Turn off the independent sources and find the form of the transient response by applying KVL and KCL.
 - Depending on the damping found, the unknown constants will be found.
3. We obtain the steady state response as:

$$x_{ss}(t) = x(\infty)$$

Where $x(\infty)$ is the final value of x obtained in step 1

Second Order Op-amp Circuits II

- 4. The total response is now found as the sum of the transient response and steady-state response.**

$$x(t) = x_t(t) + x_{ss}(t)$$

Duality

- **The concept of duality is a time saving measure for solving circuit problems.**
- **It is based on the idea that circuits that appear to be different may be related to each other.**
- **They may use the same equations, but the roles of certain complimentary elements are interchanged.**
- **The following is a table of dual pairs**

Duality

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

TABLE 8.1

Dual pairs.

Resistance R	Conductance G
Inductance L	Capacitance C
Voltage v	Current i
Voltage source	Current source
Node	Mesh
Series path	Parallel path
Open circuit	Short circuit
KVL	KCL
Thevenin	Norton

Duality

- **Once you know the solution to one circuit, you have the solution to the dual circuit.**
- **Finding the dual of a circuit can be done with a graphical method:**
 - 1. Place a node at the center of each mesh of a given circuit. Place the reference node outside the given circuit.**
 - 2. Draw lines between the nodes such that each line crosses an element. Replace the element with its dual**

Duality

- 3. To determine the polarity of voltage sources and of current sources, follow this rule: A voltage source that produces a positive (clockwise) mesh current has as its dual a current source whose reference direction is from the ground to the nonreference node.**
- When in doubt, one can refer to the mesh or nodal equations of the dual circuit.**