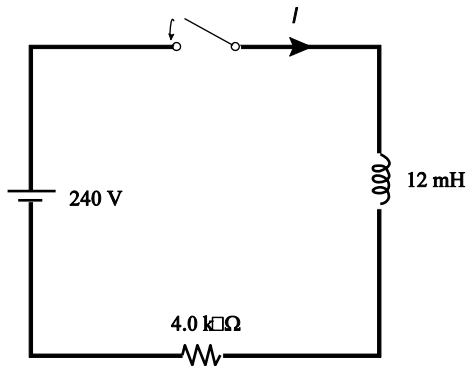


PHYS 2326 University Physics II – Class number -

QUIZ - #3  
CHAPTERS: 30,31,32,33,34

JULY 31, 2013


1. The switch in the figure is closed at  $t = 0$  when the current  $I$  is zero. When  $I = 15$  mA, what is the potential difference across the inductor?



- a. 240 V
  - b. 60 V
  - c. 0
  - d. 180 V
  - e. 190 V
2. A series LC circuit contains a 100 mH inductor, a 36.0 mF capacitor and a 12 V battery. The angular frequency of the electromagnetic oscillations in the circuit is
- a.  $36.0 \times 10^{-4}$  rad/s.
  - b.  $6.00 \times 10^{-2}$  rad/s.
  - c. 2.78 rad/s.
  - d. 16.7 rad/s.
  - e. 277 rad/s.


3. A 0.5-H inductor is connected into a 110 V-rms 60-Hz voltage source, with an ammeter in series. What is the rms value of the current through the inductor?
- 0.189 A (rms)
  - 0.292 A (rms)
  - 0.584 A (rms)
  - 1.19 A (rms)
  - 0.093 A (rms)
4. Find the resonant frequency for a series  $RLC$  circuit where  $R = 10\Omega$ ,  $C = 5\ \mu\text{F}$ , and  $L = 2\ \text{mH}$ .
- 998 Hz
  - 1.592 kHz
  - 2.45 kHz
  - 11.3 kHz
  - 2.53 kHz

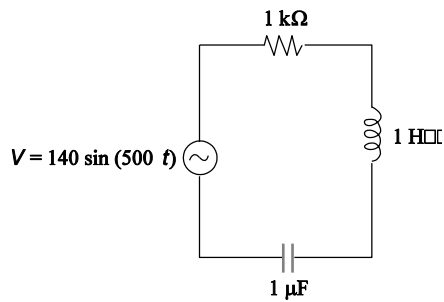5. Determine the rms voltage drop across the capacitor in the circuit.



- 55 V
- 77 V
- 110 V
- 154 V
- 198 V

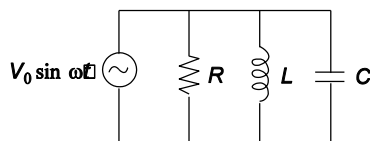**BONUS:** The phase angle between  $V$  and  $I$  is



a.  $\tan^{-1} \left[ \frac{R}{X_C} - \frac{R}{X_L} \right]$

b.  $\tan^{-1} \left( \frac{R}{X_C - X_L} \right)$

c.  $\tan^{-1} \left( \frac{X_C - X_L}{R} \right)$

d.  $\tan^{-1} \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$

e.  $\tan^{-1} \sqrt{R^2 + (X_L - X_C)^2}$

**BONUS:** If the maximum  $E$ -component of an electromagnetic wave is  $600 \text{ V/m}$ , what is the maximum  $B$ -component?

a.  $1.4 \text{ T}$

b.  $1.8 \times 10^{-5} \text{ T}$

c.  $2.0 \times 10^{-6} \text{ T}$

d.  $1.0 \times 10^{-3} \text{ T}$

e.  $1.6 \times 10^{-10} \text{ T}$

**BONUS:** Find the force exerted by reflecting sunlight off a reflecting aluminum sheet in space if the area normal to the sunlight is  $10\,000 \text{ m}^2$  and the solar intensity is  $1350 \text{ W/m}^2$ .

a.  $0.72 \text{ N}$

b.  $0.09 \text{ N}$

c.  $9 \text{ N}$

d.  $45 \text{ N}$

e.  $0.18 \text{ N}$